

Digital Logic Circuits (Spring 2026)

HW #2 (Due: April 8, 2026)

11. Apply DeMorgan's theorems to the following:

$$\begin{array}{ll} \text{(a)} \overline{\overline{ABC}(\overline{EFG}) + \overline{HIJ}(KLM)} & \text{(b)} \overline{(A + \overline{BC} + \overline{CD}) + \overline{BC}} \\ \text{(c)} \overline{(A + B)(C + D)(E + F)(G + H)} & \end{array}$$

15. Draw the logic circuit represented by each expression:

$$\begin{array}{ll} \text{(a)} AB + \overline{AB} & \text{(b)} ABCD \\ \text{(c)} A + BC & \text{(d)} ABC + D \end{array}$$

21. Using Boolean algebra, simplify the following expressions:

$$\begin{array}{ll} \text{(a)} CE + C(E + F) + \overline{E}(E + G) & \text{(b)} \overline{B}\overline{C}D + \overline{(B + C + D)} + \overline{B}\overline{C}\overline{D}E \\ \text{(c)} (C + CD)(C + \overline{C}D)(C + E) & \text{(d)} BCDE + BC(\overline{DE}) + (\overline{BC})DE \\ \text{(e)} BCD[BC + \overline{D}(CD + BD)] & \end{array}$$

33. Develop a truth table for each of the SOP expressions:

$$\text{(a)} \overline{A}B + AB\overline{C} + \overline{A}\overline{C} + \overline{A}\overline{B}C \quad \text{(b)} \overline{X} + \overline{Y}Z + WZ + \overline{X}YZ$$

42. Expand each expression to a standard SOP form:

$$\begin{array}{ll} \text{(a)} AB + \overline{A}BC + ABC & \text{(b)} A + BC \\ \text{(c)} \overline{A}\overline{B}\overline{C}D + A\overline{C}\overline{D} + B\overline{C}D + \overline{A}BC\overline{D} & \text{(d)} \overline{A}\overline{B} + \overline{A}\overline{B}\overline{C}D + CD + B\overline{C}D + ABCD \end{array}$$

43. Minimize each expression in Problem 42 with a Karnaugh map.

49. Use a Karnaugh map to simplify each expression to minimum POS form:

$$\begin{array}{ll} \text{(a)} (A + \overline{B} + C + \overline{D})(\overline{A} + B + \overline{C} + D)(\overline{A} + \overline{B} + \overline{C} + \overline{D}) & \\ \text{(b)} (X + \overline{Y})(W + \overline{Z})(\overline{X} + \overline{Y} + \overline{Z})(W + X + Y + Z) & \end{array}$$

11. Apply DeMorgan's theorems to the following:

(a) $\overline{(ABC)(EFG) + (HIJ)(KLM)}$

(b) $\overline{(A + \overline{BC} + CD) + \overline{BC}}$

(c) $\overline{(A + B)(C + D)(E + F)(G + H)}$

$\overline{BC} = \overline{B} + \overline{C}$

(a) $= \overline{(ABC)(EFG)(HIJ)(KLM)}$

$= \overline{(ABC)(EFG)(HIJ)(KLM)}$

$= (\overline{A} + \overline{B} + \overline{C}) \dots$

$= (\overline{A} + \overline{B} + \overline{C}) \dots$

$= (\overline{A} + \overline{B} + \overline{C})(\overline{E} + \overline{F} + \overline{G})(\overline{H} + \overline{I} + \overline{J})(\overline{K} + \overline{L} + \overline{M})$

(b) $= \overline{(A + \overline{B} + C + CD) + BC}$

$= \overline{(A + \overline{B} + C) + BC}$

$= \overline{B}(\overline{A} + \overline{C}) + BC$

$= BC(\overline{A} + \overline{C})$

$= BC\overline{A}\overline{C} = 0$

(c) $= \overline{(A+B)(C+D)(E+F)(G+H)}$

$= \overline{A}\overline{B}\overline{C}\overline{D}\overline{E}\overline{F}\overline{G}\overline{H}$

42. Expand each expression to a standard SOP form:

(a) $AB + \overline{A}BC + ABC$

(b) $A + BC$

(c) $\overline{A}BCD + ACD + \overline{B}CD + \overline{A}BCD$

(d) $\overline{A}B + \overline{A}\overline{B}CD + CD + \overline{B}CD + ABCD$

(a) $AB(C + \overline{C}) + \overline{A}BC + ABC$

$= ABC + \overline{A}BC + \overline{A}BC$

(b) $A(\overline{B} + B)(C + \overline{C}) + (A + \overline{A})BC$

$= ABC + \overline{A}BC + \overline{A}BC + \overline{A}BC + ABC + \overline{A}BC$

$= ABC + \overline{A}BC + \overline{A}BC + \overline{A}BC + \overline{A}BC$

(c) $\overline{A}\overline{B}CD + A(B + \overline{B})\overline{C}D + (A + \overline{A})\overline{B}CD + \overline{A}BCD$

$= \overline{A}\overline{B}CD + ABCD + \overline{A}BCD + \overline{A}BCD + \overline{A}BCD + \overline{A}BCD$

(d) $= \overline{A}B(C + \overline{C})(D + \overline{D}) + \overline{A}\overline{B}CD + (A + \overline{A})(B + \overline{B})CD$

$+ (A + \overline{A})\overline{B}CD + ABCD$

$= \overline{A}\overline{B}CD + \overline{A}\overline{B}CD + \overline{A}\overline{B}CD + \overline{A}\overline{B}CD + \overline{A}\overline{B}CD + \overline{A}\overline{B}CD + \overline{A}\overline{B}CD + \overline{A}\overline{B}CD$

$+ \overline{A}\overline{B}CD + \overline{A}\overline{B}CD + \overline{A}\overline{B}CD + \overline{A}\overline{B}CD + \overline{A}\overline{B}CD + \overline{A}\overline{B}CD$

$= ABCD + \overline{A}BCD + \overline{A}BCD + \overline{A}BCD + \overline{A}BCD + \overline{A}BCD + \overline{A}BCD + \overline{A}BCD$

$+ \overline{A}BCD + \overline{A}BCD + \overline{A}BCD$

21. Using Boolean algebra, simplify the following expressions:

(a) $CE + C(E + F) + \overline{E}(E + G)$

(b) $\overline{B}CD + (B + C + D) + \overline{B}CDE$

(c) $(C + CD)(C + \overline{C}D)(C + E)$

(d) $BCDE + BC(\overline{D}E) + (BC)DE$

(e) $BCD[BC + \overline{D}(CD + BD)]$

(a) $CE + CE + CF + 0 + \overline{E}G$

$= CE + CF + \overline{E}G$

$= C(E + F) + \overline{E}G$

(b) $\overline{B}CD + \overline{B}CD + \overline{B}CDE$

$= \overline{B}CD + \overline{B}CD$

$= \overline{B}C$

(c) $C(C + D)(C + E)$

$= C$

(d) $BC + \overline{B}CDE = BC + DE$

(e) $BCD + 0 = BCD$

33. Develop a truth table for each of the SOP expressions:

(a) $\overline{A}B + \overline{A}BC + \overline{A}\overline{C} + \overline{A}BC$

(b) $\overline{X} + Y\overline{Z} + WZ + \overline{X}YZ$

(a) $\overline{A}B = \overline{A}B(C + \overline{C})$

$= \overline{A}BC + \overline{A}B\overline{C}$

$\overline{A}\overline{C} = \overline{A}\overline{C}(B + \overline{B})$

$= \overline{A}B\overline{C} + \overline{A}\overline{B}\overline{C}$

$\overline{A}BC + \overline{A}B\overline{C} + \overline{A}B\overline{C} + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}\overline{C}$

$= \overline{A}BC + \overline{A}B\overline{C} + \overline{A}B\overline{C} + \overline{A}\overline{B}\overline{C} + \overline{A}B\overline{C}$

A	B	C	output
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

(a)

AB \ C	0	1
00	0	0
01	0	0
11	1	1
10	0	1

$AB + AC$

$= A(B + C)$

(b)

AB \ C	0	1
00	0	0
01	0	1
11	1	1
10	1	1

$BC + AB + A\overline{C} + \overline{A}B$

$= A + BC$

(b) $\bar{x} \Rightarrow x=0$

$y\bar{z} \Rightarrow y=1, \bar{z}=0$

$wz \Rightarrow w=1, z=1$

$x\bar{y}z \Rightarrow x=1, y=0, z=1$

w	x	y	z	output
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

43(c)

AB \ CD	00	01	11	10
00	0	0	0	0
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

$$\bar{B}\bar{C}D + A\bar{C}D + BC\bar{D} + AC\bar{D}$$

$$\bar{C}D(A+B) + (A+B)\bar{C}D$$

$$= (A+B)(\bar{C}D + C\bar{D})$$

43(d)

AB \ CD	00	01	11	10
00	0	0	1	0
01	0	1	1	0
11	0	1	1	0
10	1	1	1	1

$$CD + BD + A\bar{B}$$

$$= D(B+C) + A\bar{B}$$

49. Use a Karnaugh map to simplify each expression to minimum POS form:

(a) $(A + \bar{B} + C + \bar{D})(\bar{A} + B + \bar{C} + D)(\bar{A} + \bar{B} + \bar{C} + \bar{D})$

(b) $(X + \bar{Y})(W + \bar{Z})(\bar{X} + \bar{Y} + \bar{Z})(W + X + Y + Z)$

49)

① $A=0, B=1, C=0, D=1$

② $A=1, B=0, C=1, D=0$

③ $A=1, B=1, C=1, D=1$

cannot simplify

AB \ CD	00	01	11	10
00	1	1	1	1
01	1	0	1	1
11	1	1	0	1
10	1	1	1	0

(b) ① $wxyz = x01x$

② $wxyz = 0xx1$

③ $x111$

④ 0000

w+x \ y+z	00	01	11	10
00	0	0	0	0
01	1	0	0	1
11	1	1	0	1
10	1	1	0	0

$$(w+x)(\bar{y}+\bar{z})(w+\bar{z})(x+\bar{y})$$